

Lecture 16, Oct 17, 2022

Alternative Design for Example FSM

- State machine designs are not unique

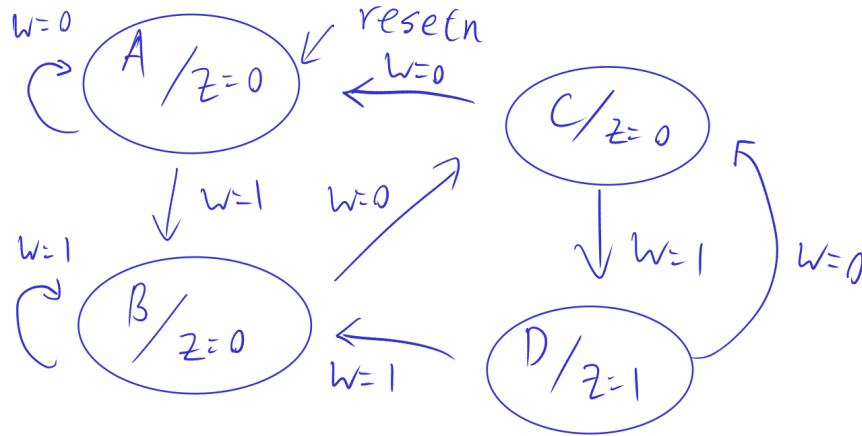


Figure 1: State diagram for the example problem

- From this state diagram we can make a state table:

State	Next $w = 0$	Next $w = 1$	z
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1

- Instead of using 2 flip flops we can use 4 flip flops $y_4y_3y_2y_1$
 - Assign state codes as $A = 0001, B = 0010, C = 0100, D = 1000$
 - This is a *one-hot encoding*, where for each state there is only 1 bit that's 1
- State-assigned table:

$y_4y_3y_2y_1$	$Y_4Y_3Y_2Y_1$ for $w = 0$	$Y_4Y_3Y_2Y_1$ for $w = 1$	z
0001	0001	0010	0
0010	0100	0010	0
0100	0001	1000	0
1000	0100	0010	1

- We can synthesize the circuit simply by inspecting the state diagram
 - Y_4 is 1 in state D ; transition to state D is from state C with $w = 1$, so $Y_4 = y_3w$
 - Similar for Y_3 : transitions are from state D with $w = 0$ and from state B with $w = 0$ so $Y_3 = (y_4 + y_2)\bar{w}$
 - For Y_2 : transitions are from A with $w = 1$, B with $w = 1$, D with $w = 1$ so $Y_2 = (y_1 + y_2 + y_4)w$
 - For Y_1 : transitions are from A with $w = 0$, C with $w = 0$ so $Y_1 = (y_1 + y_3)\bar{w}$
 - Finally $Z = y_4$
- This different circuit will produce the same behaviour as the one from the previous lecture
- We can do another alternative design in which each state represents the last 3 values of w
 - This simply produces a 3-bit shift register with a comparator
 - A shift register consists of flip-flops chained together

Verilog Code for Example FSM

- All we need to do in Verilog is to specify the state table (using a `case` statement)
- Separate the code into 3 sections:
 1. Flip-flops (reset + update to new value)
 2. State table
 3. Output

```
module fsm(input logic w, clock, resetn,  
           output logic z);  
    // Define states  
    typedef enum logic [1:0] (A, B, C, D) statetype;  
    statetype ps, ns;  
    // 1. Flip flops  
    always_ff @(posedge clock, negedge resetn)  
        if (!resetn)  
            // Make present state A on reset  
            ps <= A;  
        else  
            // Otherwise, make the present state take the next state's value  
            ps <= ns;  
    // 2. State table  
    always_comb  
        // Determine next state from the present state  
        case (ps)  
            A: ns = w ? B : A;  
            B: ns = w ? B : C;  
            C: ns = w ? D : A;  
            D: ns = w ? B : C;  
        endcase  
    // 3. Assign output  
    assign z = (ps == D);  
endmodule
```

- `enum` defines an *enumeration*, which makes the compiler encode the state for us
 - The type after `enum` is the underlying type, in this case a 2-bit logic value
 - The symbols in brackets after are the possible values for the enum; in this case we can refer to the states now as *A, B, C, D*
 - By default, these are in numerical order, but the compiler sees this only as a suggestion (if it can optimize by changing the encodings, then it will do so)
- `typedef <type> <name>` defines a type alias, in this case `statetype` for the enum type